



Tutorial 2: VHDL Design and Simulation

Tutor Notes

1 Introduction

The aim of this tutorial is to provide you with experience in VHDL design and simulation by implementing various building blocks which are used for microprocessor interfacing. These include a decoder and a latch. All of these designs will first be simulated using Altium Designer before downloading to the NanoBoard for implementation. The DIP switches and TEST/RESET button will be used as inputs and the LEDs will be used as outputs. As an additional task, the bi-directional octal register described in lectures can be simulated.

Each design should be implemented as a separate FPGA project. Parts of the design from one project can be copied to the next. The detailed procedure for the decoder, which should also be followed for the latch is:

The students are given a procedure for creating their design for simulation. There seems to be a problem with the VHDL test bench creation from the schematic, which is why another way for creating the test bench is described. This procedure should be the basis for all their design work in the future. Once thing that has not been mentioned here, but may be elaborated later, is that it is possible to have many test benches in a design, with each test bench testing a different part. This may be useful when doing the laboratory project.

- Follow example from the previous tutorial to start a new FPGA project in a new directory and create blank schematic.
- This time a sheet symbol will be created first which will include the VHDL code for the decoder. Create a sheet symbol by using **Place** → **Sheet Symbol** on the schematic view.
- Edit the *Filename* parameter of the symbol to be the name of your choice (for example *Decoder3to8.Vhd*). The template VHDL file will be this name and the root name will be used as the entity name.
- You also need to add the parameter *VHDLENTITY* to the symbol to match the entity name in the VHDL code by selecting the symbol and using the pull-down menu to select the **Properties...** option.
- To add inputs and outputs to the sheet (ports), use **Place** → **Add Sheet Entry** and place them as required. Edit the names and types by selecting the port and using the **Properties...** menu option. The decoder requires a bus with three signals as an input and a bus with eight signals as an output.
- Place the DIPSWITCH part to be used as the input and the LED part to be used as the output. Connect these to the sheet symbol that was created above. The input will require a bus joiner to connect only three of the DIPSWITCH signals to the decoder.
- Create a template VHDL file by selecting the sheet symbol created above and using **Sheet Symbol Actions** → **Create VHDL File from Symbol**. Rename the VHDL file to an appropriate name by using the **Save as ...** menu option.

Note: Alternatively, the VHDL file can be written first and a sheet symbol created from it. Doing it this way, the *Filename* and the *VHDLENTITY* parameters are set automatically. The method you use is your choice.

- Write the VHDL code for the decoder in the template VHDL file. You will also want to include the following two lines for the libraries:

```
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
```

The use of the IEEE library has to be enabled for the project. Select **Project** → **Project Options...** and click on the **Synthesis** tab. Select the **Include IEEE Numeric STD Library** check box and close the window. However, this should not be required if using the Altium synthesiser.

- To simulate the design a VHDL test bench is required. Normally, an option to create a VHDL test bench from the top-level schematic should work, however it is proving problematic.
- This is the alternative method for creating a VHDL test bench. First select **Simulator** → **HDL Compile** and fix any possible compilation errors. Once this is done, find the generated VHDL file which represents the top level schematic in the **Projects** view under **Generated / VHDL Files**. Open this VHDL file and select **Design** → **Create VHDL Testbench**. This will create a template file for stimulus code to be inserted. You may want to include extra libraries as required at the top of the file.
- The top level of the simulation is the test bench. Select **Project** → **Project Options...** again and click on the **Simulation** tab. Fill in the details in the **Design** area to match the test bench for the design and close the window.
- Start the simulation by selecting **Simulator** → **Simulate**. Click **Done** on the pop up window and start the simulation using **Simulator** menu with the appropriate **Run** command.
- Follow the example from the previous tutorial for downloading the design to the NanoBoard. Remember that the project has to be configured to target the FPGA on the NanoBoard.

Be careful not to name projects, sheets and VHDL files and entities with the same name as this can cause problems with the software. As always, refer to the in-line documentation. A convenient method is to use the search function to locate specific information.

One more thing. When a symbol has a bus input or output (such as the decoder input and output) don't use individual wires but rather a bus. The notation for a bus on a schematic is *name[from..to]* where *name* is the name of the bus, *from* is the number of the first signal and *last* is the name of the last signal (for example, the decoder input could be labelled *a[2..0]* which refers to three signals).

2 Decoder

- Create a new FPGA project and design a three-to-eight decoder, which each of the outputs high for a particular combination of the input. Connect three of the DIP switches to the input and connect the outputs to the LEDs.

A decoder is designed to only have one of its outputs asserted based on the input combination. The truth table for a three to eight decoder is shown in Table 1. In this case the output is active high, that is, the decoded value has logic level 1

Input			Output							
a_2	a_1	a_0	q_7	q_6	q_5	q_4	q_3	q_2	q_1	q_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Table 1: Truth table for a three to eight decoder

while all other outputs are at logic level 0. This could be referred to as positive logic. An alternative would be to have the decoded output at logic level 0 while all the other outputs are at logic level 1. This could be referred to as negative logic.

A schematic of the decoder as it would appear in a schematic diagram is shown in Figure 1. This forms the basis for the entity declaration as all the inputs and outputs are shown.

There are a number of ways that the decoder can be described. Two possible ways are shown starting on Page 8. The template was deleted to make the code more compact. The first example used `ieee.std_logic_unsigned.all` which allows the input to be compared to an unsigned number. The second example used `ieee.numeric_std.all` which includes the type casting function. Either way is fine. It was suggested in lectures just to include both of these libraries.

 


Figure 1: Schematic of a three to eight decoder

I have given instructions above on how to use Altium Designer to do the design. I don't want to go into too much detail. The best thing would be for you to help the students with their designs as necessary. The schematic used entered in the Altium software should be similar to that shown in Figure 2. Note that the DIP switch inputs are flipped around and the

 


Figure 2: Schematic of the three to eight decoder showing the DIP switch inputs and the LED outputs

last three are used to make it easier to operate.

In each of the above examples, the entity declaration is the same, only the architecture changes.

- b) Simulate the design by creating a VHDL test bench and using the Altium Designer Simulator. Test all input combinations and verify correct operation. If the simulation does not provide the expected results, modify the design and repeat the simulation.

A test bench for the decoder is shown on Page 9. The bulk of this code is generated automatically by Altium Designer, only the stimulus needs to be added. The result of the simulation is shown in Figure 3. In this simulation, all the input combinations are tested to show correct operation. Note that the extra label was added to the schematic to view the input

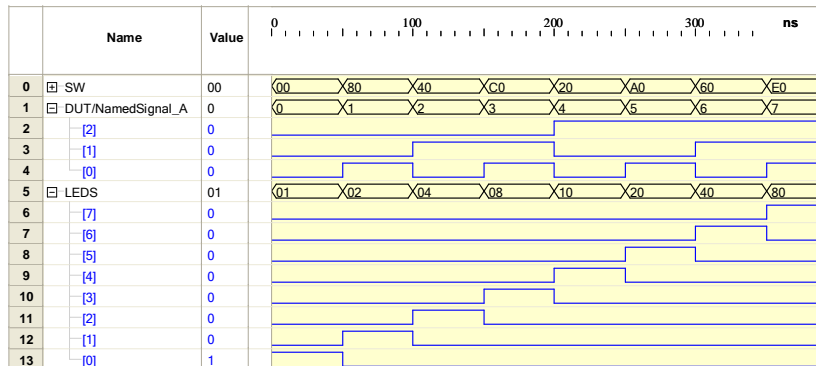


Figure 3: Simulation of the three to eight decoder

in a meaningful way.

Students should not download their designs until it is running correctly in simulation. You may want to point out to them that the turn around time for simulation is far quicker than that for implementation to the NanoBoard.

- c) Download the design to the NanoBoard and verify that the design operates as predicted in the simulation.

Need to configure for use with the FPGA on the NanoBoard are done in the previous tutorial. This should be a straight forward step and will confirm that the design operates as simulated.

- d) If the decoder is used to decode the top three bits of an eight-bit address space, what are the addresses corresponding to each of the decoder outputs?

The total number of addresses for an eight bit address space is $2^8 = 256$. If the top three bits were decoded, the address range corresponding to that output would start from the top three bit combination with the lower five bits set to zero and finish at the top three bit combination with the lower five bits set to one. Note that the output of the decoder does not change with changes on the lower five bits. This is completely obvious as none of the lower five bits are inputs to the decoder.

The easiest way to describe the answer is to write an address map. This is shown in Table 2. In this table, the address bits

Output $q_7 \rightarrow q_0$	Address Bits							Range		
	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0	Start	Finish
q_0	0	0	0	X	X	X	X	X	00	1f
q_1	0	0	1	X	X	X	X	X	20	3f
q_2	0	1	0	X	X	X	X	X	40	5f
q_3	0	1	1	X	X	X	X	X	60	7f
q_4	1	0	0	X	X	X	X	X	80	9f
q_5	1	0	1	X	X	X	X	X	a0	bf
q_6	1	1	0	X	X	X	X	X	c0	df
q_7	1	1	1	X	X	X	X	X	e0	ff

Table 2: Address map for decoding the top three bits in an eight bit address space

are labelled A_7 down to A_0 . The top three bits are fed into the decoder to generate the decoded output. The X's are used to show that this bit can take on either value. The address range as a start and finish address is shown in the last column. The number of addresses that each output decodes is $2^5 = 32$.

3 Latch

- a) Create a new FPGA project and design a positive edge-triggered three-input latch. Connect three of the DIP switches to the input and connect the outputs to three of the LEDs. Use the TEST/REST button as the clock input. Do not worry about debouncing the clock input.

A schematic for the latch is shown in Figure 4.

 


Figure 4: Schematic of a three input latch

In this case, a process statement with a sensitivity on the clock input ck is used. The VHDL code for this is shown on Page 11. This is a subset of the code that was presented in lectures for a bi-directional octal register. Note that the d input is not included in the sensitivity list.

The schematic used is similar to that for the decoder only that there is now an extra input for the TEST/RESET button. The actual schematic should be similar to that shown in Figure 5. Note that the DIP switch inputs was flipped around and the last three were used to make it easier to operate.

 


Figure 5: Schematic of the three input latch showing the DIP switch and TEST/RESET button inputs and the LED outputs

- b) Simulate the design by creating a VHDL test bench and using the Altium Designer Simulator. Verify correct operation and fix if necessary.

The test bench is shown on Page 11. The simulation of the design is shown in Figure 6. The edge on the clock at which

 


Figure 6: Simulation of the latch

the output is latched is determined by the conditional if statement which explicitly looks for a change in state of the clock input and what state it goes to. A good example of an elegant solution using VHDL.

- c) Download the design to the NanoBoard and verify that the design operates as predicted in the simulation.

This should be straight forward.

- d) Create a new FPGA project to include the latch connected to the decoder. Connect three of the DIP switches to the input of the latch and connect the outputs of the decoder to the LEDs. Simulate to verify correct operation and then download the design to the NanoBoard.

This is just a combination of the two. It may be possible to create a part to put in a library and then place it on the new sheet. Otherwise, create the part from the VHDL file as before. Try different ways of doing it until you find one that works well to tell the students. The schematic is shown in Figure 7. The simulation uses the same test bench stimulus as that used for the latch. The simulation results is shown in Figure 8. Note that the latch output is undefined until the first positive edge of the clock input.

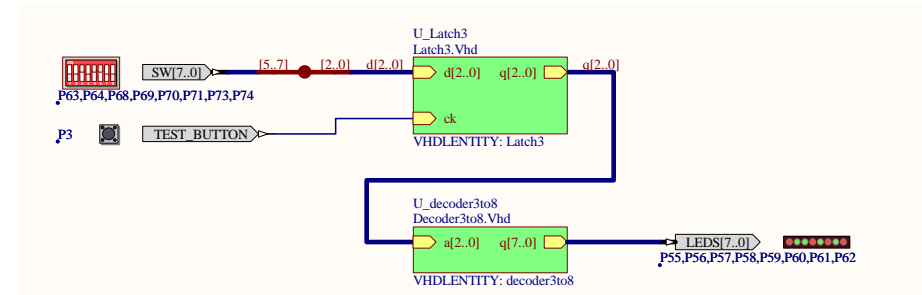


Figure 7: Schematic of the three input latch connected to the decoder

 


Figure 8: Simulation of the three input latch connected to the decoder

4 Bi-Directional Octal Register

This task is optional. Create a new FPGA project and implement the bi-directional octal register as described in lectures. Simulate the design for all possible combinations of direction and output-enable signals. Take care when changing the direction signal as the new output has to be driven to high impedance.

This question is optional for the students who are keen to experiment with the simulator. The design of the bi-directional octal register was given in lectures. Schematically, the register and some internal detail is shown in Figure 9. This is a good example where a VHDL description is far more concise and simple than a schematic diagram.

The VHDL code is provided on the ELEC4605 web site to save having to type it in. It is also shown on Page 13.

The schematic from Altium Designer is shown in Figure 10.

The simulation result is shown in Figure 11 given the test bench on Page 13. This is a good example to try changing what signals appear in the process statement sensitivity list.

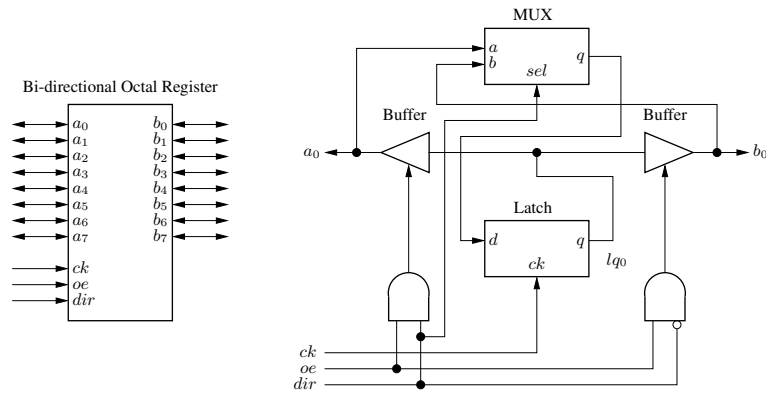


Figure 9: Schematic of the bi-directional octal register at left with some internal detail at right

 


Figure 10: Schematic of the three input latch connected to the decoder

 


Figure 11: Simulation of the octal register with output enable and direction

VHDL Code

Decoder - Example 1

— ELEC4605 Computer Engineering
 — Decoder3to8.vhd
 — Example 1: Using std_logic_unsigned package
 — Peter Stepien
 — 2005

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity decoder3to8 is
    port(a : in std_logic_vector(2 downto 0);
         q : out std_logic_vector(7 downto 0));
end decoder3to8;
```

```
architecture behaviour of decoder3to8 is
begin
    q(0) <= '1' when a=0 else '0';
    q(1) <= '1' when a=1 else '0';
    q(2) <= '1' when a=2 else '0';
    q(3) <= '1' when a=3 else '0';
    q(4) <= '1' when a=4 else '0';
    q(5) <= '1' when a=5 else '0';
    q(6) <= '1' when a=6 else '0';
    q(7) <= '1' when a=7 else '0';
end behaviour;
```

Decoder Example 2

— ELEC4605 Computer Engineering
 — Decoder3to8.vhd
 — Example 2: Using numeric_std package
 — Peter Stepien
 — 2005

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity decoder3to8 is
    port(a : in std_logic_vector(2 downto 0);
         q : out std_logic_vector(7 downto 0));
end decoder3to8;
```

```
architecture behaviour of decoder3to8 is
begin
    q(0) <= '1' when unsigned(a)=0 else '0';
    q(1) <= '1' when unsigned(a)=1 else '0';
    q(2) <= '1' when unsigned(a)=2 else '0';
    q(3) <= '1' when unsigned(a)=3 else '0';
    q(4) <= '1' when unsigned(a)=4 else '0';
    q(5) <= '1' when unsigned(a)=5 else '0';
    q(6) <= '1' when unsigned(a)=6 else '0';
    q(7) <= '1' when unsigned(a)=7 else '0';
end behaviour;
```

Decoder Test Bench

```

— VHDL Testbench for Decoder
— 2005 3 16 15 12 39
— Created by "EditVHDL"
— "Copyright (c) 2002 Altium Limited"

```

```

Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_textio.all;
Use STD.textio.all;

```

```

entity TestDecoder is
end TestDecoder;

```

```

architecture stimulus of TestDecoder is
  file RESULTS: TEXT open WRITE_MODE is "results.txt";
  procedure WRITE_RESULTS(
    LEDES: std_logic_vector(7 downto 0);
    SW: std_logic_vector(7 downto 0)
  ) is
    variable l_out : line;
  begin
    write(l_out, now, right, 15);
    write(l_out, LEDES, right, 9);
    write(l_out, SW, right, 9);
    writeline(RESULTS, l_out);
  end procedure;

  component Decoder
    port (
      LEDES: out std_logic_vector(7 downto 0);
      SW: in std_logic_vector(7 downto 0)
    );
  end component;

  signal LEDES: std_logic_vector(7 downto 0);
  signal SW: std_logic_vector(7 downto 0);

begin
  DUT: Decoder port map (
    LEDES => LEDES,
    SW => SW
  );

  STIMULUS0: process
  begin
    — insert stimulus here
    SW <= b"00000000"; wait for 50ns;
    SW <= b"10000000"; wait for 50ns;
    SW <= b"01000000"; wait for 50ns;
    SW <= b"11000000"; wait for 50ns;
    SW <= b"00100000"; wait for 50ns;
    SW <= b"10100000"; wait for 50ns;
    SW <= b"01100000"; wait for 50ns;

```

```

    SW <= b"11100000"; wait for 50ns;
    wait;
  end process;

  WRITE_RESULTS(
    LEDES,
    SW
  );
end architecture;

```

Latch

```

— ELEC4605 Computer Engineering
— Latch3.Vhd
— Peter Stepien
— 2005

```

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Latch3 is
  port(ck : in std_logic;
        d : in std_logic_vector(2 downto 0);
        q : out std_logic_vector(2 downto 0));
end;

architecture behaviour of Latch3 is
begin
  process (ck)
  begin
    if (ck='1' and ck'event) then
      q <= d;
    end if;
  end process;
end;

```

Latch Test Bench

```

— VHDL Testbench for Latch
— 2005 3 17 11 57 40
— Created by "EditVHDL"
— "Copyright (c) 2002 Altium Limited"

```

```

Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_textio.all;
Use STD.textio.all;

```

```

entity TestLatch is
end TestLatch;

```

```

architecture stimulus of TestLatch is
  file RESULTS: TEXT open WRITE_MODE is "results.txt";
  procedure WRITE_RESULTS(
    LEDS: std_logic_vector(7 downto 0);
    SW: std_logic_vector(7 downto 0);
    TEST_BUTTON: std_logic
  ) is
    variable l_out : line;
  begin
    write(l_out, now, right, 15);
    write(l_out, LEDS, right, 9);

```

```

    write(l_out, SW, right, 9);
    write(l_out, TEST_BUTTON, right, 2);
    writeline(RESULTS, l_out);
  end procedure;

  component Latch
  port (
    LEDS: out std_logic_vector(7 downto 0);
    SW: in std_logic_vector(7 downto 0);
    TEST_BUTTON: in std_logic
  );
  end component;

  signal LEDS: std_logic_vector(7 downto 0);
  signal SW: std_logic_vector(7 downto 0);
  signal TEST_BUTTON: std_logic;

begin
  DUT: Latch port map (
    LEDS => LEDS,
    SW => SW,
    TEST_BUTTON => TEST_BUTTON
  );

  STIMULUS0: process
  begin
    — insert stimulus here
    TEST_BUTTON <= '0';
    — Latch b"000"
    SW <= b"00000000"; wait for 25ns;
    TEST_BUTTON <= '1'; wait for 25ns;
    TEST_BUTTON <= '0'; wait for 25ns;
    — Latch b"010"
    SW <= b"01000000"; wait for 25ns;
    TEST_BUTTON <= '1'; wait for 25ns;
    TEST_BUTTON <= '0'; wait for 25ns;
    wait;
  end process;

  WRITE_RESULTS(
    LEDS,
    SW,
    TEST_BUTTON
  );
end architecture;

```

Bi-directional Octal Register

```

— ELEC4605 Computer Engineering
— Reg8OEDIR.Vhd
— Peter Stepien
— 2005

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity reg8oedir is
    port(ck, oe, dir : in std_logic;
         a           : inout std_logic_vector(7 downto 0);
         b           : inout std_logic_vector(7 downto 0));
end;

architecture behaviour of reg8oedir is
    signal lq : std_logic_vector(7 downto 0);
begin

    Latch: process (ck)
    begin
        if (ck='1' and ck'event) then
            if dir='0' then
                lq <= a;
            elsif dir='1' then
                lq <= b;
            end if;
        end if;
    end process;

    — Output_Enable
    b <= lq when ((oe='1') and (dir='0')) else "ZZZZZZZ";
    a <= lq when ((oe='1') and (dir='1')) else "ZZZZZZZ";

end;

```

Bi-directional Octal Register Test Bench

```

— VHDL Testbench for BiDirRegister
— 2005 3 17 13 50 46
— Created by "EditVHDL"
— "Copyright (c) 2002 Altium Limited"

Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_textio.all;
Use STD.textio.all;

```

```

entity TestBiDirRegister is
end TestBiDirRegister;

```

```

architecture stimulus of TestBiDirRegister is
    file RESULTS: TEXT open WRITE_MODE is "results.txt";
    procedure WRITE_RESULTS(
        A: std_logic_vector(7 downto 0);
        B: std_logic_vector(7 downto 0);
        CK: std_logic;
        DIR: std_logic;
        OE: std_logic
    ) is
        variable l_out : line;
    begin
        write(l_out, now, right, 15);
        write(l_out, A, right, 9);
        write(l_out, B, right, 9);
        write(l_out, CK, right, 2);
        write(l_out, DIR, right, 2);
        write(l_out, OE, right, 2);
        writeline(RESULTS, l_out);
    end procedure;

    component BiDirRegister
        port (
            A: inout std_logic_vector(7 downto 0);
            B: inout std_logic_vector(7 downto 0);
            CK: in std_logic;
            DIR: in std_logic;
            OE: in std_logic
        );
    end component;

    signal A: std_logic_vector(7 downto 0);
    signal B: std_logic_vector(7 downto 0);
    signal CK: std_logic;
    signal DIR: std_logic;
    signal OE: std_logic;

begin
    DUT: BiDirRegister port map (
        A => A,
        B => B,
        CK => CK,
        DIR => DIR,
        OE => OE
    );

    STIMULUS0: process
    begin
        — insert stimulus here
        dir <= '0';
        oe <= '1';
        ck <= '0';
        a <= "ZZZZZZZ";
        b <= "ZZZZZZZ";
        wait for 500ns;

        — Latch a value
        a <= b"10001000"; wait for 500ns;
        ck <= '1'; wait for 500ns;
        ck <= '0'; wait for 500ns;

        — Latch another value but disable output first

```

```
oe <= '0';
a <= b"01000100"; wait for 500ns;
ck <= '1'; wait for 500ns;
ck <= '0'; wait for 500ns;
oe <= '1';

— Latch another value
a <= b"01010101"; wait for 500ns;
ck <= '1'; wait for 500ns;
ck <= '0'; wait for 500ns;

— Change direction
dir <= '1';
a <= "ZZZZZZZ";
b <= "ZZZZZZZ";
wait for 500ns;

— Latch a value
b <= b"10001000"; wait for 500ns;
ck <= '1'; wait for 500ns;
ck <= '0'; wait for 500ns;

— Latch another value but disable output first
oe <= '0';
b <= b"01000100"; wait for 500ns;
ck <= '1'; wait for 500ns;
ck <= '0'; wait for 500ns;
oe <= '1';

— Latch another value
b <= b"01010101"; wait for 500ns;
ck <= '1'; wait for 500ns;
ck <= '0'; wait for 500ns;

    wait;
    end process;

    WRITE_RESULTS(
        A,
        B,
        CK,
        DIR,
        OE
    );

end architecture;
```